

EE6320 RF Integrated Circuits

Project: VCO Design

VCO Performance Summary Table

Design Parameter	Design Metric	Performance	Specification
Output Amplitude (V _{pp} /2)	freq = 5.17 GHz	0.9072 V	≥ 0.8V
	freq = 5.245 GHz	0.9288 V	≥ 0.8V
	freq = 5.32 GHz	0.9340 V	≥ 0.8V
Phase Noise (1 MHz Offset)	freq = 5.17 GHz	-131.46 dBc/Hz	≤ -118 dBc/Hz
	freq = 5.245 GHz	-130.98 dBc/Hz	≤ -118 dBc/Hz
	freq = 5.32 GHz	-128.88 dBc/Hz	≤ -118 dBc/Hz
Phase Noise (20 MHz Offset)	freq = 5.17 GHz	-159.20 dBc/Hz	≤ -150 dBc/Hz
	freq = 5.245 GHz	-159.30 dBc/Hz	≤ -150 dBc/Hz
	freq = 5.32 GHz	-158.12 dBc/Hz	≤ -150 dBc/Hz
Tuning Range	Total Tuning Range	510.93 MHz	≥ 150 MHz
	Number of bits in coarse tuning	5	-
	Voltage range in fine tuning	400 mV	-
	Average KVCO	142.6 MHz/V	150 MHz/V
	% variation in KVCO	31.55 %	minimal
Power Consumption (5.245 GHz)	VCO average power consumption (excluding bias)	6.6156 mW	minimal
	Bias circuit	9 mW	minimal
Other	Sum of all capacitances (in capacitor bank)	930 fF	-
	Net inductance used	800 pH	-
	Simulator used	Cadence Virtuoso	-


Name: ANIRUDH B S

Roll No: EE21B019

Component Values Table

<u>Component</u>	<u>Value</u>
Current Mirror MOS	W = 1 μm , L = 360 nm
Tail MOS	W = 1 μm , L = 360 nm
Tail Capacitance	10 μF
Tail Tank	L = 100 pH, C = 10 μF
Cross Coupled MOS(s)	W = 1 μm , L = 200 nm
Capacitor Bank	Co = 15 fF (5 binary weighted capacitors)
Varactor MOS	W = 1 μm , L = 200 nm
Drain Tank	L = 350 pH, C = 1 pF
(V bias, I bias)	Vbias = 1.2 V, Ibias = 7.5 mA

Schematic

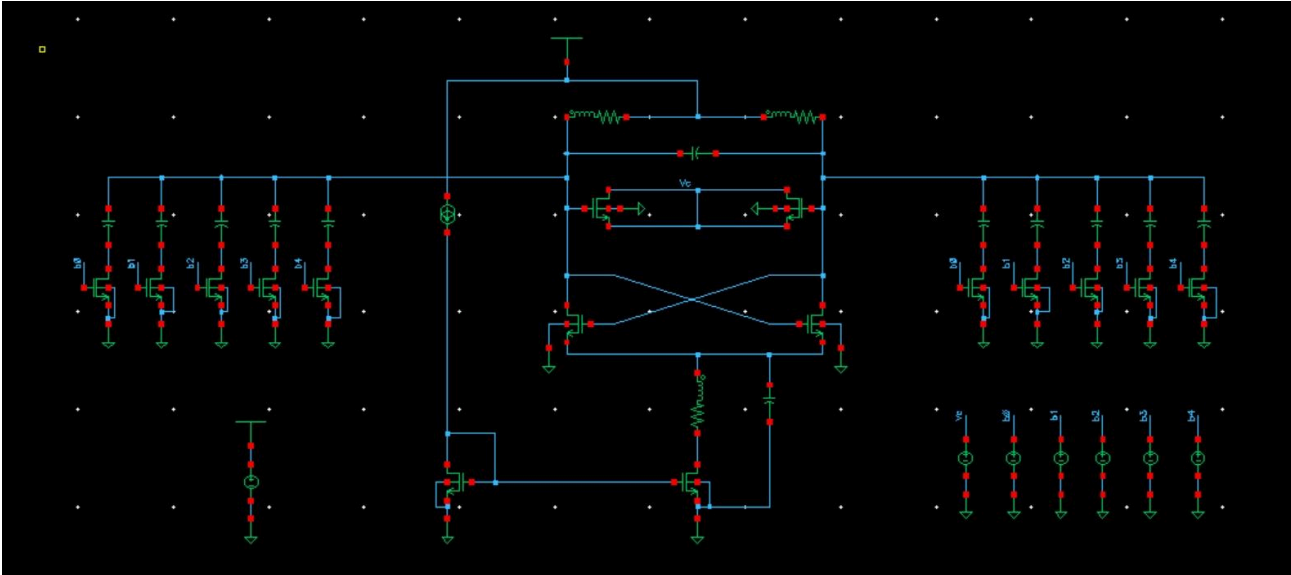

ADE L (2) - VCO VCO schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Calibre Help

cadence

Design Variables

Name	Value
1. Co	15f
2. VC	900m
3. B0	0
4. B1	1.2
5. B2	0
6. B3	1.2
7. B4	0
8. Lt	100p
9. Ld	350p
10. Cd	1p
11. Ib	7.5m
12. mv	120
13. mc	75
14. mx	10

Analyses

Type	Enable	Arguments
1. pss	<input type="checkbox"/>	10 /net14 /net15
2. pnoise	<input type="checkbox"/>	10 100K 30M 100 /net14 /net15
3. tran	<input checked="" type="checkbox"/>	0 100n


Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1. harm=1 freq: pss (Hz)		<input type="checkbox"/>	<input type="checkbox"/>	
2. output noise: dBc/Hz		<input type="checkbox"/>	<input type="checkbox"/>	
3. v /net14; tran (V)		<input type="checkbox"/>	<input type="checkbox"/>	
4. average(deriv(harmoni...		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5. v (/net14 /net15); tran (V)		<input type="checkbox"/>	<input type="checkbox"/>	
6. v /net15; tran (V)	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	


Plot after simulation: Auto Plotting mode: Replace

24(47) Save State ... Status: Ready T=27 C Simulator: spectre_aps State: SubmissionState


Output Amplitude Plots
(differential settled waveforms)
At 5.17 GHz

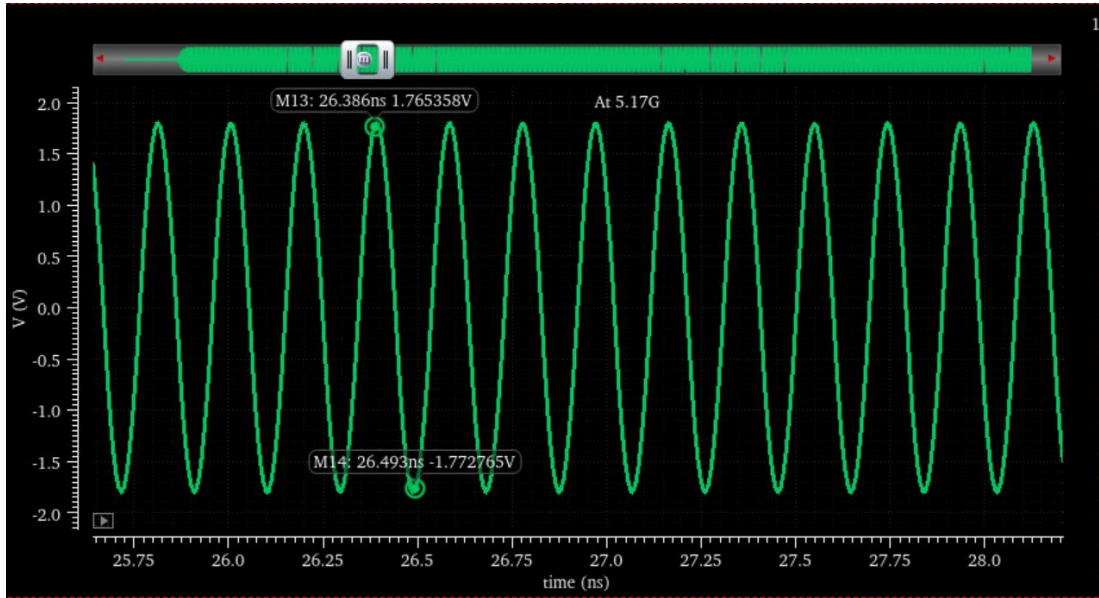

At 5.245 GHz

 


At 5.32 GHz

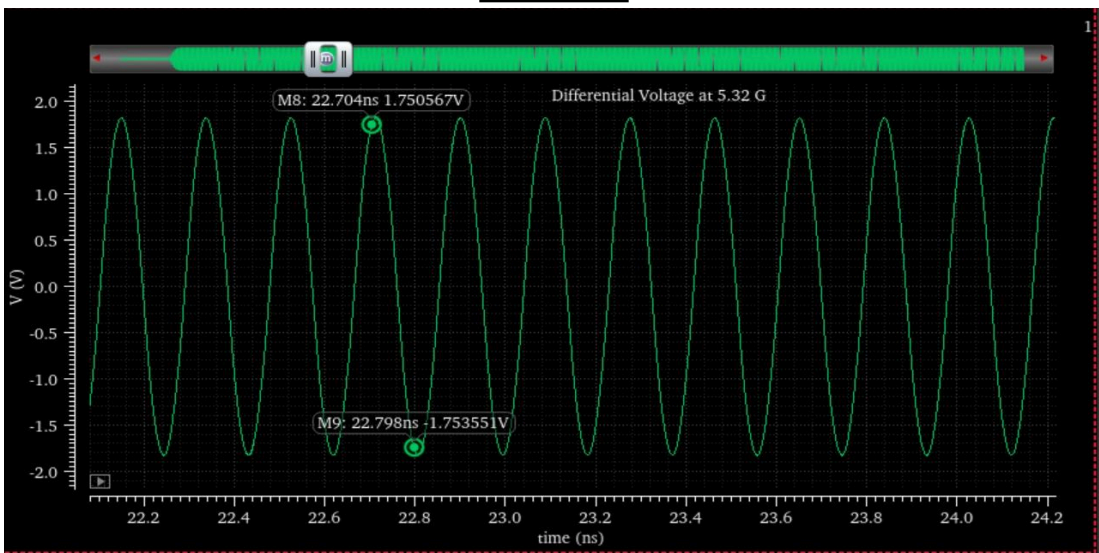


Phase Noise Plots
(at 1 MHz and 20 MHz)


At 5.17 GHz

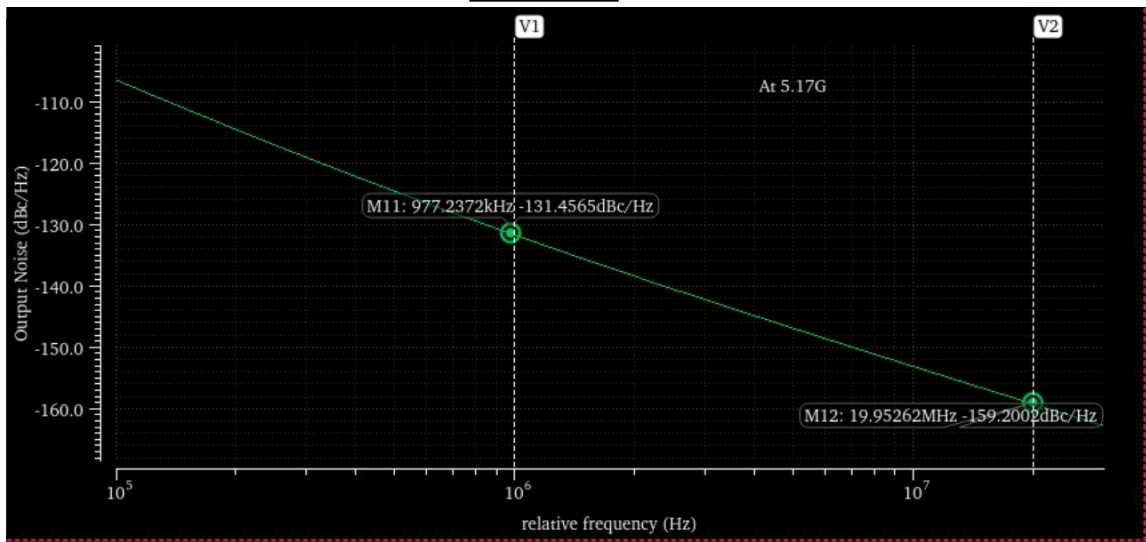


At 5.245 GHz

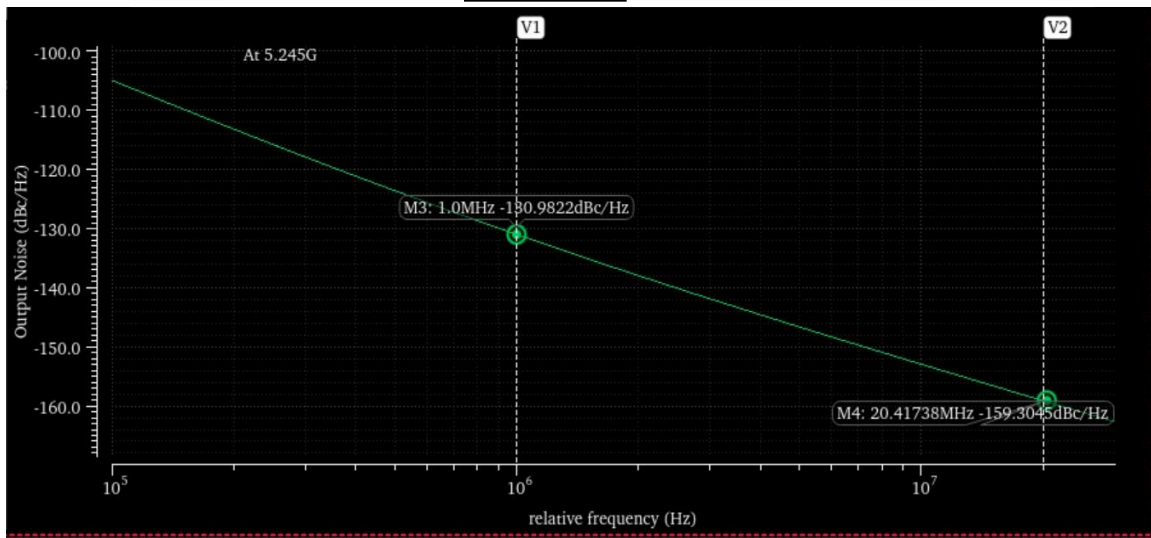

At 5.32 GHz

 

Frequency Tuning Range Plot

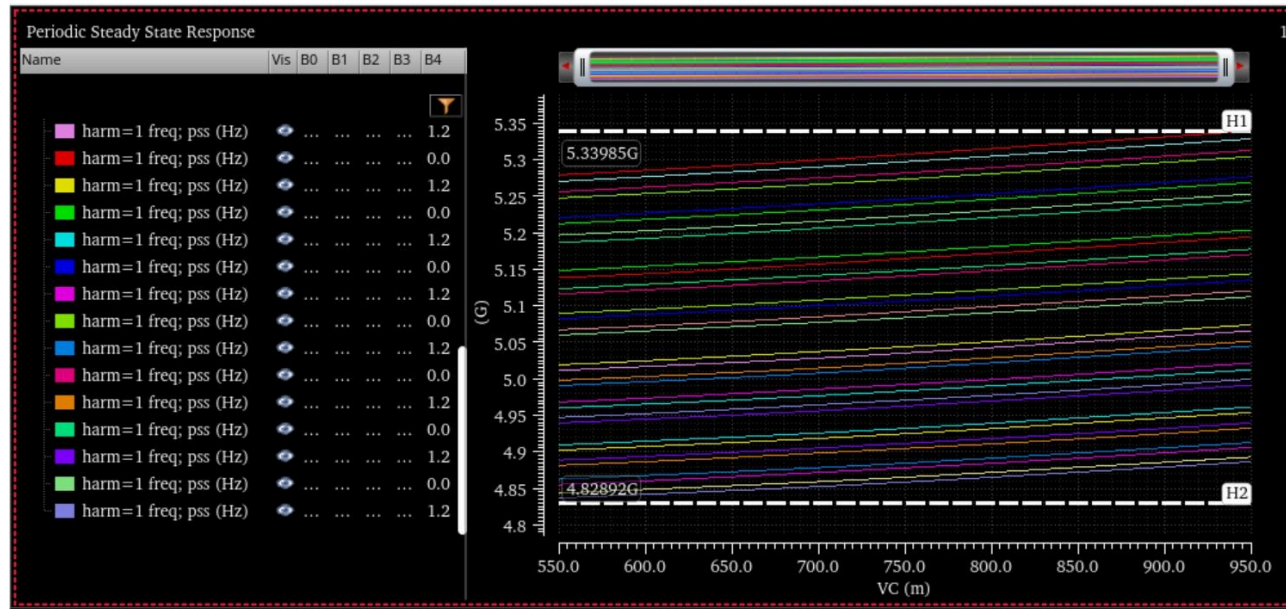

KVCO Plot

 


Fig 1 : Average KVCO = 150.4 MHz/V for B0 = B1 = B2 = B3 = B4 = 0

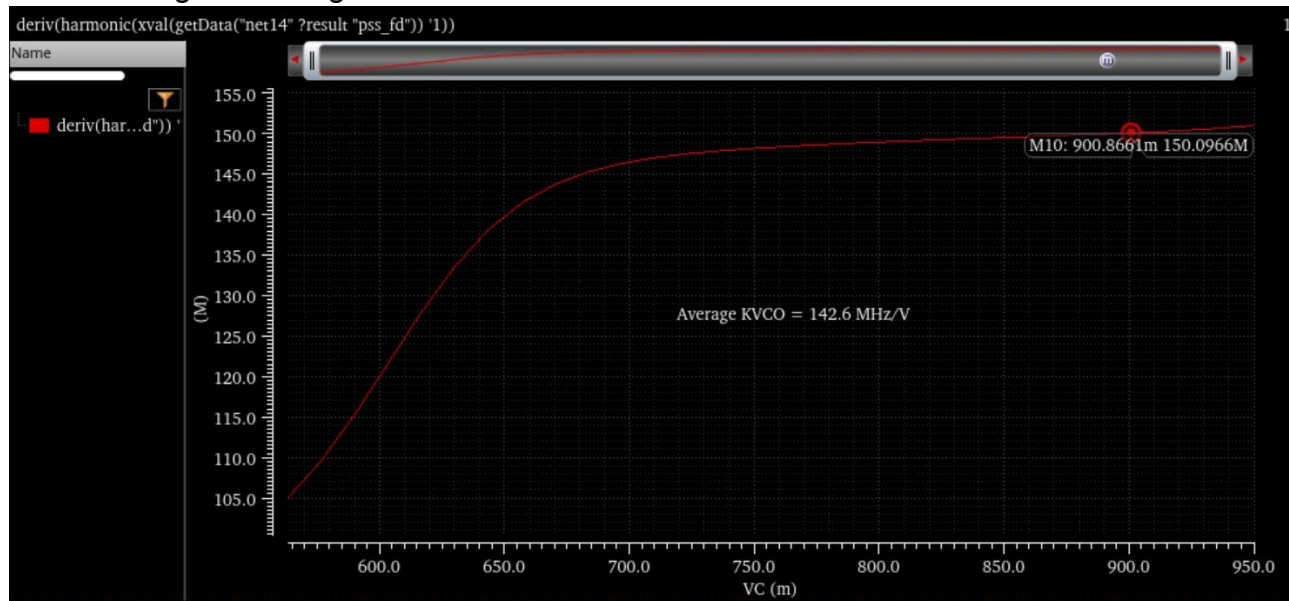


Fig 2 : Average KVCO = 142.6 MHz/V for B0 = B1 = B2 = 1.2, B3 = B4 = 0
(For 5.245GHz at Vc = 900 mV)

Overlap in Coarse Tuning Plots

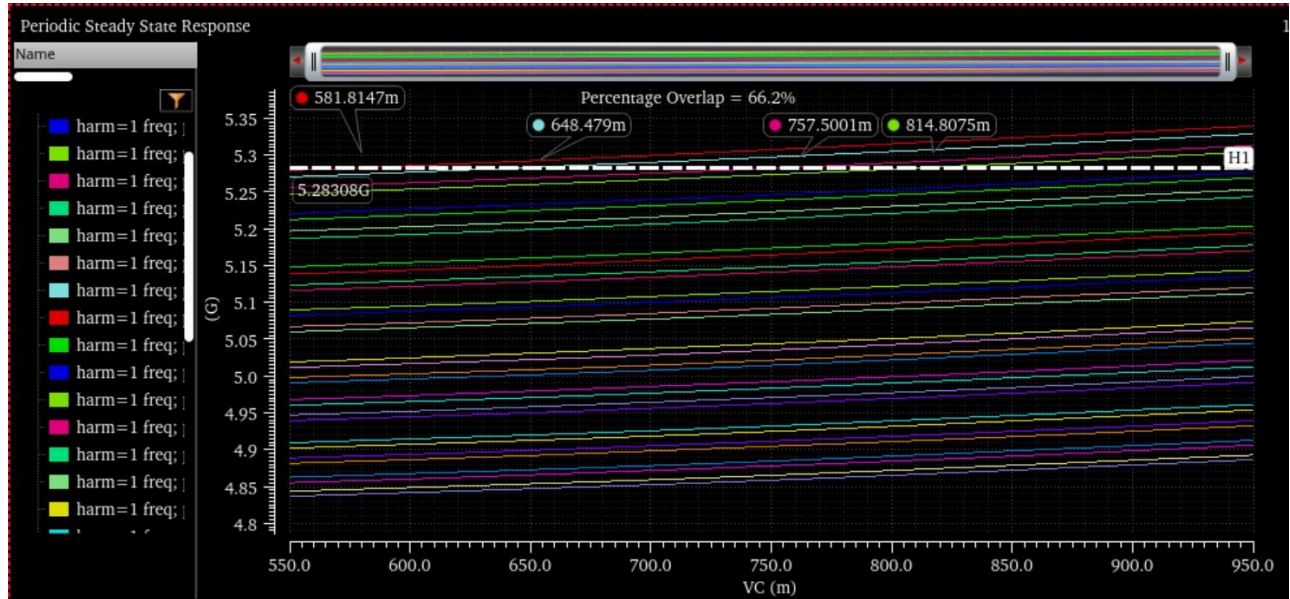


Fig 1 : Overlap between adjacent curves is 66.2%

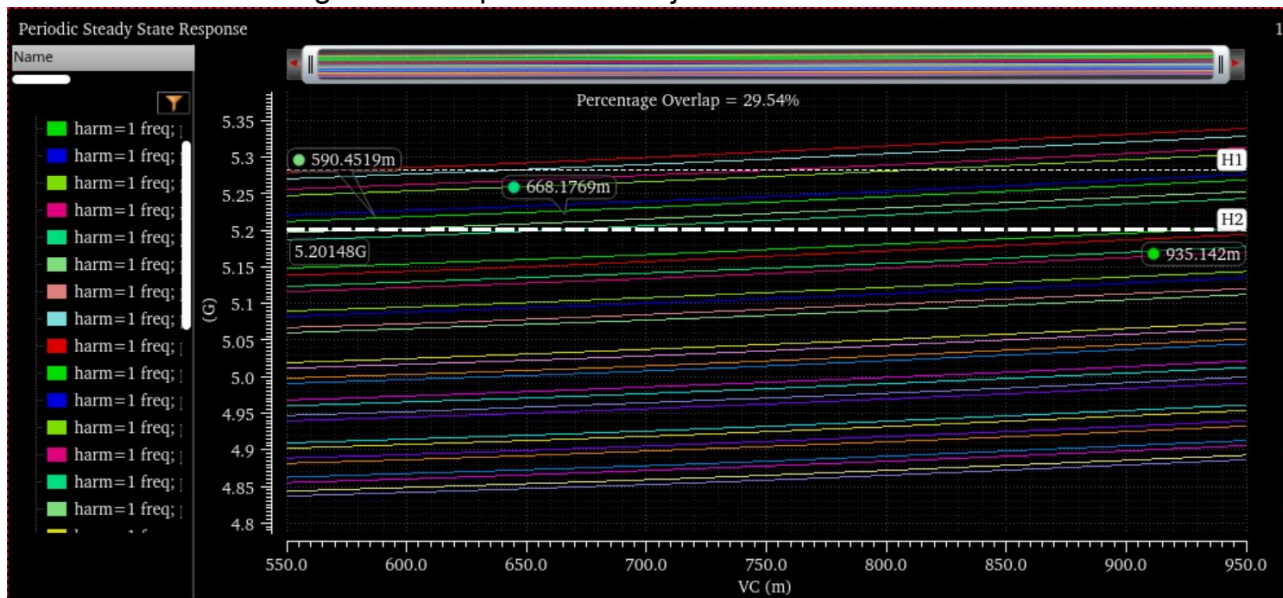


Fig 2 : Overlap between adjacent curves is 29.54%



 


Fig 3 : Overlap between adjacent curves is 33.99%

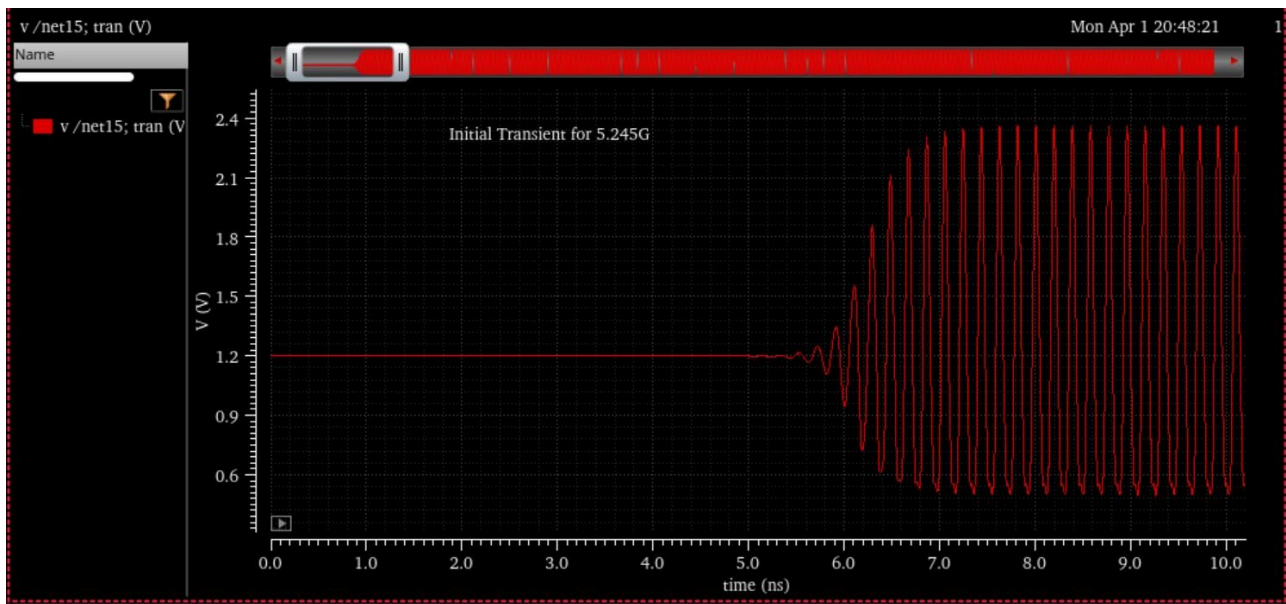Initial Transient Response Plot (for Vop at 5.245 GHz)



 Single Ended Output Plot (Vop & Von) (at 5.245 GHz)




Design Procedure

1. Hand Calculations were performed to find the initial starting point of design
2. Using the hand calculations, the simulation was performed. Specifications were not met.
3. The varactor multiplier and the cross coupled MOS multiplier was adjusted to get required KVCO. Using Ld and Cd the required frequency tuning range was attained.
4. Lt was picked to reject higher order harmonics.
5. The architecture chosen involved capacitor banks for coarse tuning and MOS based varactor for fine tuning. This was chosen so as to have more flexibility over the voltage ranges needed to be attained.
6. The overlap specification of 33% was almost attained on an average.

EEG320: RF Integrated Circuits

VCO Design

Hand Calculations

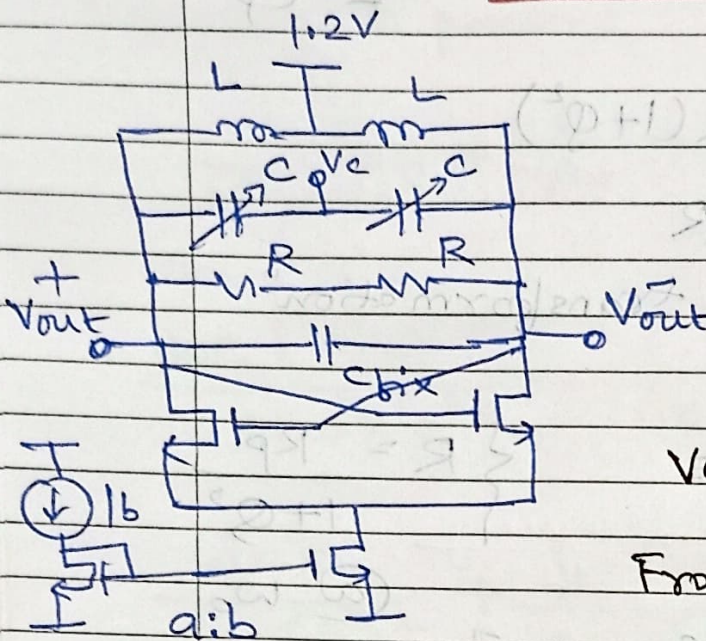

Specifications

$f_0: 5.17 \text{ GHz to } 5.32 \text{ GHz}$

$V_{DD} = 1.2 \text{ V}$

VCO single ended $\geq 0.8 \text{ V}$ output

From Fourier series,

$$\frac{2}{\pi} I_t R \geq 0.80$$

We will keep $\frac{2}{\pi} I_t R = 1$

$$\text{So that } I_t R \geq \frac{\pi}{2}$$

Single side Analysis

$$\frac{1}{\sqrt{LC_{\max}}} = 2\pi \times 5.17 \times 10^9$$

$$\Rightarrow C_{\max} = 3.79069 \text{ pF} \\ \text{@ } L = 250 \text{ pH.}$$

$$\frac{1}{\sqrt{LC_{\min}}} = 2\pi \times 5.32 \times 10^9$$

$$\Rightarrow C_{\min} = 3.58 \text{ pF} \\ \text{@ } L = 250 \text{ pH.}$$

$$C_{\max} = C_{\min} + \sum C_i$$

$$\Rightarrow \sum C_i = (1 + 2 + 4 + 8 + 16) C_0 \\ = 31 C_0$$

Date: Page:

$$31C_0 = 0.21069 \text{ pF}$$

$$\Rightarrow \boxed{C_0 = 6.796 \text{ fF}}$$

$$R = 20 \times (5.245 \times 2\pi \times 10^9) \times 0.25 \times 10^{-9}$$
$$= 164.776 \Omega$$

$$\Rightarrow \boxed{I_t \geq 9.532 \text{ mA.}}$$